
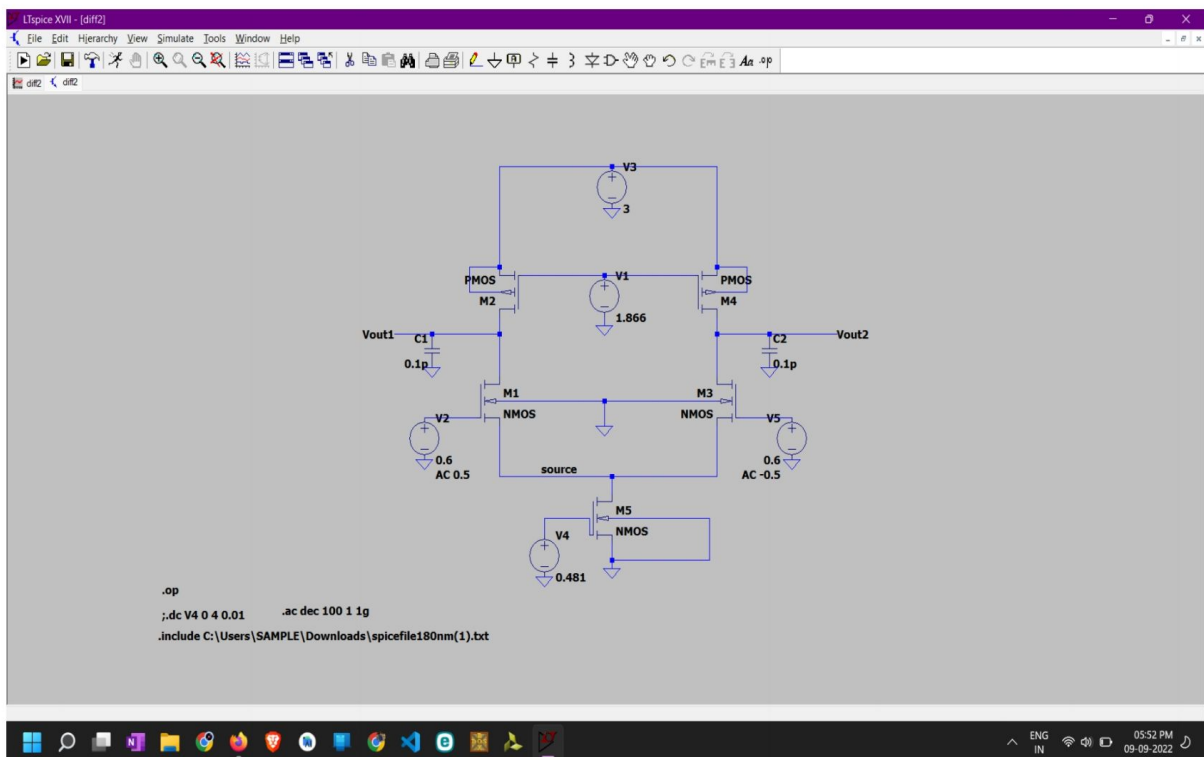


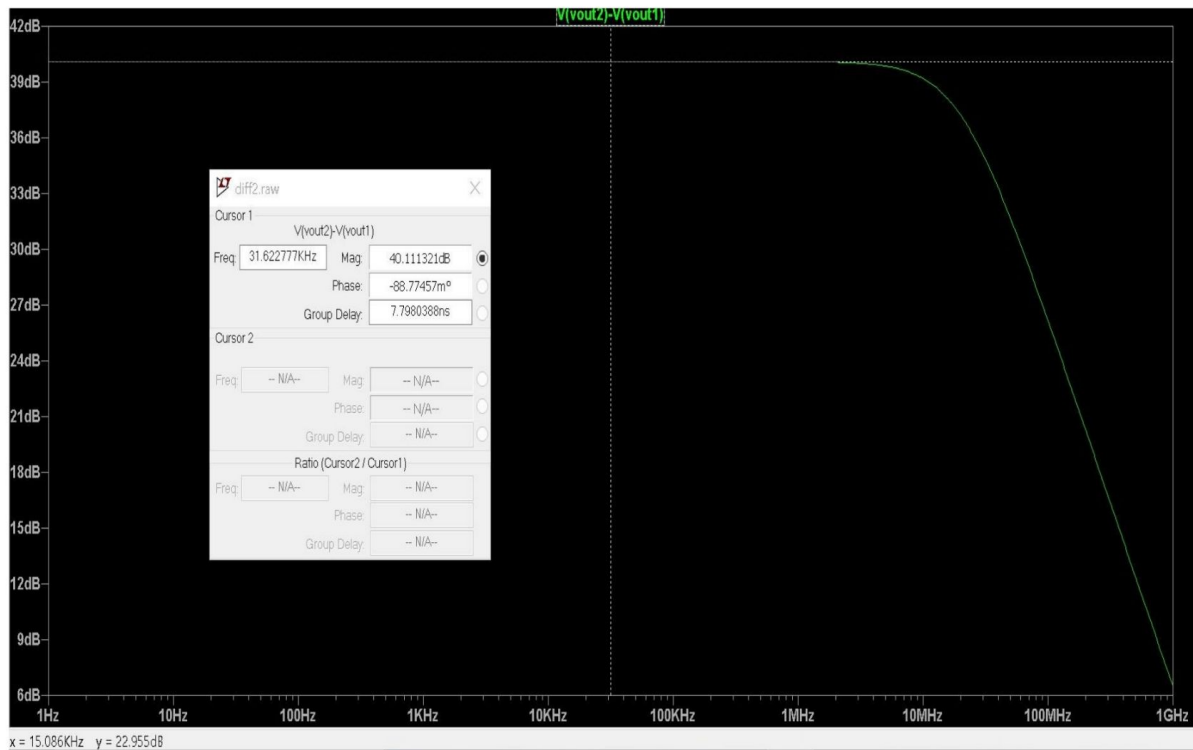
QUESTION:

Design a differential amplifier with minimum gain 40dB with nmos input pair and pmos current source load . Sum of widths of all the transistors should not exceed 1000u meter. At the input as well as output, connect a 0.1pF(100fF) capacitor. Find the bandwidth of the amplifier.





Gain of the circuit= 40.111321dB

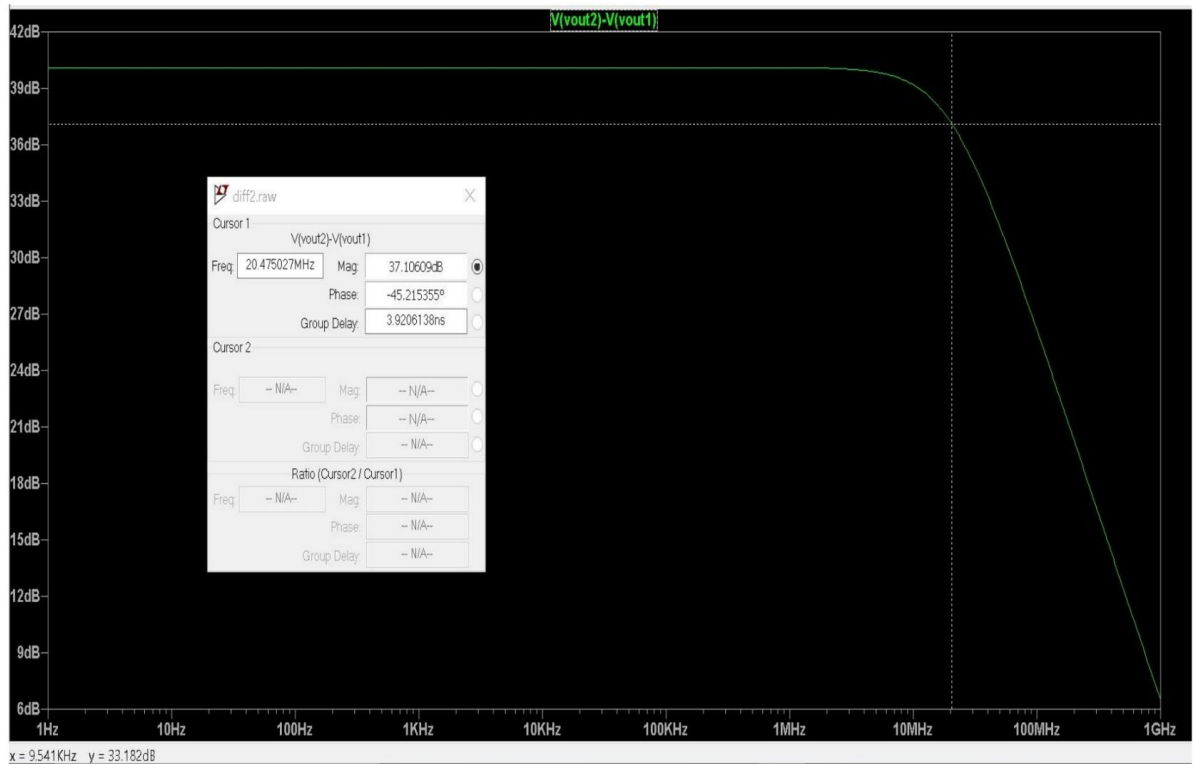

Bandwidth of the circuit= 20.475MHz

Values:

Mosfet characteristics:

parameter	M1 (NMOS) Input	M2 (PMOS) Load	M3 (NMOS) Input	M4 (PMOS) Load	M5 (NMOS) tail source
Length	0.72um	1.8um	0.72um	1.8um	1.8um
Width	180um	22.5um	180um	22.5um	522um
K_n'	44.7mA/v ²	-	44.7mA/v ²	-	0.615m
K_p'	-	43.5uA/v ²	-	43.5uA/v ²	-
V _{ov}	0.004v	0.716v	0.004v	0.716v	0.056v

Differential amplifier characteristics:

<u>Parameter</u>	<u>Values</u>
Total width of all mosfets	927um
V bias of pmos current source	1.866V
V _{dd}	3V
Gain	40.111db (101.28)
3db Bandwidth	20.47MHz

..... **THANK YOU**